

Timer

- The 555 timer is a highly stable device for generating accurate time delay or oscillation.
- A single 555 timer can provide time delay ranging from microseconds to hours whereas counter timer can have a maximum timing range of days.
- The 555 timer is versatile and easy to use in various applications. Various applications include oscillator, pulse generator, ramp and square wave generator, mono-shot multivibrator, burglar alarm, traffic light control and voltage monitor etc.


① Description of functional diagram

- Fig gives the functional diagram for 555 IC timer.
- In fig, three $5\text{ k}\Omega$ internal resistors act as voltage divider, providing bias voltage of $(2/3)V_{CC}$ to the upper comparator and $(1/3)V_{CC}$ to the lower comparator (LC), where V_{CC} is the supply voltage, since these two voltages fix the necessary comparator threshold voltage, they also aid in determining the timing interval.
- It is possible to vary time electronically too, by applying a modulation voltage to the control voltage input terminal (Pin 5).
- In applications, where no such modulation is intended, it is recommended by manufacturers that a capacitor ($0.01\text{ }\mu\text{F}$) be connected between control voltage terminal (Pin 5) and ground to by-pass noise or ripple from the supply.
- Output of the upper comparator (VC) is applied to Reset (R) input of the flip-flop. Whenever the threshold voltage exceeds the control voltage, the output of the upper comparator goes high, and the output $\bar{Q}$ of the flip-flop (FF) is High.
- A high output ^{of $\bar{Q}$} from the flip-flop saturates the discharge transistor and discharge the capacitor connected externally to pin 7.
- The complementary signal out of the flip-flop goes to pin 3, the output ~~because~~ of power amplifier is basically an inverter.


- The output available at pin 3 is low. These conditions will persist until ~~comparator~~ Low Comparator (LC) triggers the flip-flop. If the voltage at the threshold input falls below $+\left(\frac{2}{3}\right)V_{CC}$ i.e., V_C cannot cause the flip-flop to change again. It means that the V_C can only force the flip-flop's output high of $\bar{Q}$.
- To change the output of $\bar{Q}$ of flip-flop to low, the voltage at the trigger input must fall below $+\left(\frac{1}{3}\right)V_{CC}$. When this occurs, LC triggers the flip-flop, forcing its output ~~low~~ of $\bar{Q}$ low.
- The low output from the flip-flop turns the discharge transistor off and forces the power amplifier to output a high.
- These conditions will continue, independent of the voltage on the trigger input. LC can only cause the flip-flop to output low.

[Note : From the above discussion it is concluded that for the having low output from the timer 555, the on the threshold input must exceeds the control voltage or $+\frac{2}{3}V_{CC}$. The also turns the discharge transistor on. To force the output from the timer high, the voltage on the trigger input must drop below $+\frac{1}{3}V_{CC}$. This also turns the discharge transistor off.]

- The reset input (pin 4) provides a mechanism to reset the FF in a manner which overrides the effect of any instruction coming to FF from lower comparator (LC). This overriding reset is effective when the reset input is less than about 0.4V.
- When this reset is not used, it is returned to V_{CC} .
- The transistor Q_2 serves as a buffer to isolate the reset input from the FF and transistor Q_1 .
- The transistor Q_2 is driven by an internal reference voltage V_{ref} obtained from supply voltage V_{CC} .

 

Note

 

R	S	Q	Q̄
0	0	Last value return/no change	
0	1	1	0
1	0	0	1
1	1	undefined/invalid	



B 462968

Monostable Operation

- Fig shows a 555 timer connected for monostable operation.
- In the standby (stable) state, the output $\bar{Q}$ of the control flip-flop is high that is FF holds transistor Q_1 on, thus clamping the external timing capacitor C to ground.
- The output remains at ground potential, i.e. Low.
- As the trigger passes through $V_{cc}/3$, the FF is set, i.e., $\bar{Q} = 0$. This makes the transistor Q_1 off and the short circuit across the timing capacitor C is released.
- As $\bar{Q}$ is Low, Output goes High ($= V_{cc}$).
- The timing cycle now begins.
- Since C is unclamped, voltage across it rises exponentially through R towards V_{cc} with a time constant RC .
- After a time period T , the capacitor voltage is just greater than $(2/3)V_{cc}$ and the upper comparator resets the FF, that is, $R = 1, S = 0$ (assuming very small trigger pulse width).
- This makes $\bar{Q} = 1$, transistor Q_1 goes on (i.e. saturation), thereby discharging the capacitor C rapidly to ground potential.
- The output returns to the Standby state or ground potential.
- The voltage across the capacitor at any instant during charging is given as

$$V_c = V_{cc} (1 - e^{-T/RC})$$

Substituting $V_c = \frac{2}{3} V_{cc}$ in above eqⁿ. we get the time taken by the capacitor to charge from 0 to $\frac{2}{3} V_{cc}$

Therefore,
$$\frac{2}{3} V_{cc} = V_{cc} (1 - e^{-T/RC})$$

$$T = -RC \ln(1/3)$$

$$T = 1.1 RC \text{ (seconds).} \quad \text{--- (1)}$$

→ It is evident from eqⁿ (1) that the timing interval is independent of supply voltage.

→ It may also be noted that once triggered, the output remains in the High state until time T elapses, which depends only upon R and C .

→ Any additional trigger pulse coming during this time will not change the output state.

→ However, if a negative going reset pulse as in fig is applied to the reset terminal (Pin 4) during the timing cycle, transistor Q_2 goes off, Q_1 becomes on and the external timing capacitor C is immediately discharged.

→ The output now will be as in fig,

→ It may be seen that the output of Q_2 is connected directly to the input of Q_1 , so as to turn on Q_1 immediately and thereby avoid the propagation delay through the FF.

→ Now, even if the reset is released, the output will still remain Low until a negative going trigger pulse is again applied at pin 2.

 


Fig:- Monostable multivibrator

 


Fig:- Timing pulses.

Astable Operation

- The device is connected for astable operation as shown in fig.
- Comparing with monostable operation, the timing resistor is now split into two sections R_A and R_B .
- Pin 7 of discharging transistor Q is connected to the junction of R_A and R_B .
- When the power supply V_{CC} is connected, the external timing capacitor C charges towards V_{CC} with a time constant $(R_A + R_B)C$.
- During this time, output (pin 3) is high (equal to V_{CC}) as Reset R_{20} , Set $S=1$ and this combination makes $\bar{Q}=0$ which has unclamped the timing capacitor C .
- When the capacitor voltage equals (to be precise is just greater than) $\frac{2}{3}V_{CC}$ the upper comparator triggers the control flip-flop so that $\bar{Q}=1$.
- This, in turn, makes transistor Q_1 on and capacitor C starts discharging towards ground through R_B and transistor Q_1 , with a time constant $R_B C$ (neglecting the forward resistance of Q_1).
- Current also flows into transistor Q_1 through R_A . Resistors R_A and R_B must be large enough to limit this current and prevent damage to the discharge transistor Q_1 .
- The minimum value of R_A is approximately equal to $V_{CC}/0.2$ where 0.2 is the maximum current through the on transistor Q_1 .
- During the discharge of the timing capacitor C , as it reaches (to be precise, is just less than) $\frac{1}{3}V_{CC}$, the lower comparator is triggered and at this stage $S=1$, R_{20} , which turns $\bar{Q}=0$. Now $\bar{Q}=0$ unclamps the external timing capacitor C .
- The capacitor C is thus periodically charged and discharged between $(\frac{2}{3})V_{CC}$ and $(\frac{1}{3})V_{CC}$ respectively.
- Fig. shows the timing sequence and capacitor voltage waveform.
- The length of time that the output remains High is the time for the capacitor to charge from $(\frac{1}{3})V_{CC}$ to $(\frac{2}{3})V_{CC}$.
- It may be calculated as follows:

The Capacitor voltage for a low pass RC circuit subjected to a step input of V_{cc} volts is given by

$$V_c = V_{cc}(1 - e^{-T/RC})$$

The time T_1 taken by the circuit to change from 0 to $(2/3)V_{cc}$

$$(2/3)V_{cc} = V_{cc}(1 - e^{-T_1/RC})$$

$$\text{or, } T_1 = 1.09 RC$$

and the time T_2 to change from 0 to $(1/3)V_{cc}$ is

$$(1/3)V_{cc} = V_{cc}(1 - e^{-T_2/RC})$$

$$\text{or, } T_2 = 0.405 RC$$

So, the time to change from $(1/3)V_{cc}$ to $(2/3)V_{cc}$ is

$$T_{HIGH} = T_1 - T_2 = 0.69 RC$$

So, for the given circuit,

$$T_{HIGH} = 0.69 (R_A + R_B) C$$

The output is low while the capacitor discharges from $(2/3)V_{cc}$ to $(1/3)V_{cc}$ and the voltage across the capacitor is given by

$$(1/3)V_{cc} = (2/3)V_{cc} e^{-T/RC}$$

$$\text{Solving, we get } T = 0.69 RC$$

$$\text{So, for the given circuit, } T_{LOW} = 0.69 R_B C$$

Notice that both R_A and R_B are in the charge path, but only R_B is in the discharge path. Therefore, total time,

$$T = T_{HIGH} + T_{LOW}$$

$$\text{or, } T = 0.69 (R_A + 2R_B) C$$

$$\text{So, } f = \frac{1}{T} = \frac{1.45}{(R_A + 2R_B) C}$$

$$\text{and Duty cycle, } D = \frac{T_{ON}}{T_{ON} + T_{OFF}} \times 100\%$$

 


Fig:- Astable multivibrator using 555 timer.

 


Fig: Timing sequence of astable multivibrator.